



The number of diodes in the regulator circuit is different depending on the type of analysis:

- 17 diodes on Octave's theoretical analysis
- 23 diodes on NGSpice's simulation analysis